

23 CAPACITORS

23.1 Capacitance

	a	b	c	d	
1.) Q (nC)	6.0	330	9900	6.30	Using $C = \frac{Q}{V}$
V (V)	12	2.2	9.0	4.5	
C (μF)	5.0	150	1100	1.4	

2. a) $Q = V \times C = 12.0 \times 22 \times 10^{-6} = \underline{2.64 \times 10^{-4} \text{ C}}$

b) $Q = I \times t \rightarrow 2.64 \times 10^{-4} = 2.5 \times 10^{-6} \times t$
 $\text{time} = \frac{2.64 \times 10^{-4}}{2.5 \times 10^{-6}} = \underline{106 \text{ s}}$

3 a) $Q = I \times t = 0.5 \times 10^{-6} \times 55 = \underline{2.75 \times 10^{-5} \text{ C}}$

b) $C = \frac{Q}{V} = \frac{2.75 \times 10^{-5}}{5} = \underline{5.5 \times 10^{-6} \text{ F}} \text{ or } 5.5 \mu\text{F}$

4. a) $Q = I \times t = 24 \times 10^{-6} \times 38 = \underline{9.12 \times 10^{-4} \text{ C}} \rightarrow 9.12 \text{ nC, not } 9.12 \mu\text{C (textbook)}$

b) $C = \frac{Q}{V} = \frac{9.12 \times 10^{-7}}{4.2} = \underline{2.2 \times 10^{-7} \text{ F}} \text{ or } 0.22 \mu\text{F}$

c) $Q_2 = I_2 \times t_2 = 14 \times 10^{-6} \times 50 = \underline{7.0 \times 10^{-4} \text{ C}}$

d) $C = \frac{Q}{V}$ (same C, so use 2.2×10^{-7}) $\rightarrow 2.2 \times 10^{-7} = \frac{7.0 \times 10^{-4} + 9.1 \times 10^{-4}}{V}$
 $\hookrightarrow V = \underline{7.4 \text{ V}}$

23.2 Energy stored in a charged capacitor

1. a) $Q = V \times C = 3.0 \times (10 \times 10^{-6}) = 3.0 \times 10^{-5} \text{ C}$
 $E = \frac{1}{2} CV^2 = \frac{1}{2} (10 \times 10^{-6}) \times 3^2 = \underline{4.5 \times 10^{-5} \text{ J}}$

b) $Q = V \times C = 6.0 \times (10 \times 10^{-6}) = 6.0 \times 10^{-5} \text{ C}$
 $E = \frac{1}{2} CV^2 = \frac{1}{2} (10 \times 10^{-6}) \times 6^2 = \underline{1.8 \times 10^{-4} \text{ J}}$


2. a) $Q = V \times C = 9 \times 50,000 \times 10^{-6} = \underline{0.45 \text{ C}}$
 $E = \frac{1}{2} CV^2 = \frac{1}{2} (50,000 \times 10^{-6}) \times 9^2 = \underline{2.0 \text{ J}}$

b) $P = E \div t = 2.0 / 0.2 = \underline{10 \text{ W}}$

23.2

3. a) i) $Q = V \times C = 3 \times (2.2 \times 10^{-6}) = \underline{6.6 \times 10^{-6} \text{ C}}$
 $E = \frac{1}{2} CV^2 = \frac{1}{2} \times (2.2 \times 10^{-6}) \times 3^2 = \underline{9.9 \times 10^{-6} \text{ J}}$

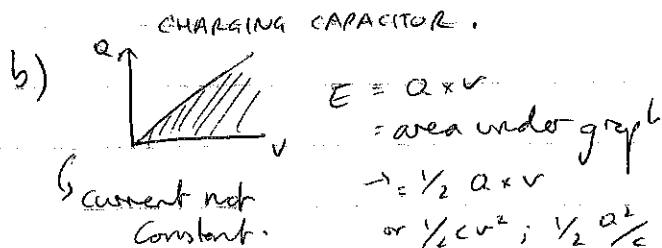ii) $Q = V \times C = \underline{6.6 \times 10^{-6} \text{ C}}$ (same as 3. ai)
 $E = CV^2 = [ai] \times 2 = 9.9 \times 10^{-6} \times 2 = \underline{19.8 \times 10^{-6} \text{ J}}$



50% of energy supplied is wasted as thermal energy (lost resistance) ~~in capacitor~~

4. a) Initial charge, $Q = V \times C = 12.0 \times 4.7 \times 10^{-6} = \underline{5.64 \times 10^{-5} \text{ C}}$
 $E = \frac{1}{2} CV^2 = \frac{1}{2} \times (4.7 \times 10^{-6}) \times 12^2 = \underline{3.38 \times 10^{-4} \text{ J}}$

b) Total charge available $Q_T = \underline{5.64 \times 10^{-5} \text{ C}}$

i) $Q_1 + Q_2 = 5.64 \times 10^{-5} \text{ C}$ Total p.d. = 12V is same in each Capacitor [parallel circuit]

$\frac{Q}{C} = V \rightarrow$ for each capacitor,
 $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} = 12$

Ratios of capacitors $\rightarrow 2.2 \mu\text{F} : 4.7 \mu\text{F}$ (Total = $6.9 \mu\text{F}$)


$\therefore$ ratio charges $\rightarrow \left(\frac{2.2}{6.9} \times 5.64 \times 10^{-5} \right) = \underline{18 \mu\text{C}}$

$\rightarrow \left(\frac{4.7}{6.9} \times 5.64 \times 10^{-5} \right) = \underline{36 \mu\text{C}}$

ii) final p.d, $V = \frac{Q_{\text{Total}}}{C_{\text{Total}}} = \frac{5.64 \times 10^{-5}}{(2.2 + 4.7)} = \underline{8.2 \text{ V}}$

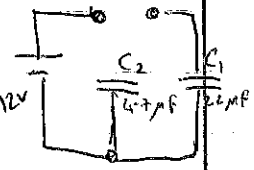c) $E_1 = \frac{1}{2} C_1 V^2 = \frac{1}{2} \times 2.2 \times 10^{-6} \times 8.2^2 = \underline{7.3 \times 10^{-5} \text{ J}}$

$E_2 = \frac{1}{2} C_2 V^2 = \frac{1}{2} \times (4.7 \times 10^{-6}) \times 8.2^2 = \underline{1.57 \times 10^{-4} \text{ J}}$



23.3 Charging and discharging a Capacitor through a fixed resistor

1. a) i) $Q = V \times C = 6 \times (50 \times 10^{-6}) = \underline{\underline{3.0 \times 10^{-4} \text{ C}}}$

ii) Time constant $= R \times C = (100 \times 10^3) \times (50 \times 10^{-6}) = \underline{\underline{5 \text{ s}}}$

b) $\frac{2V}{6V} = 33\%$ of its original value.

time constant $= 5 \text{ s}$ to decrease to e^{-1} or 37%
 $\rightarrow$ so it will be $\sim \underline{\underline{5 \text{ s}}}$ (slightly longer)

ii) $\frac{V}{V_0} = e^{-\frac{t}{RC}} \rightarrow \text{time constant}$

$0.01 = e^{-\frac{5}{RC}} \rightarrow \ln 0.01 = \frac{5}{R \times (50 \times 10^{-6})}$
 $\rightarrow 99\% \text{ discharged, } 1\% \text{ left}$

$R = \underline{\underline{22,000 \Omega}}$

2. a) i) $Q = V \times C = 9.0 \times (68 \times 10^{-6}) = \underline{\underline{6.12 \times 10^{-4} \text{ C}}}$

ii) $V = I \times R \rightarrow 9.0 = I \times 20 \times 10^3 \rightarrow I = \underline{\underline{4.5 \times 10^{-4} \text{ A}}}$

b) $V = V_0 e^{-\frac{t}{R}} = 9 \times e^{-\frac{5}{(20,000 \times 68 \times 10^{-6})}}$
 $= \underline{\underline{0.228 \text{ V}}}$

$I = \frac{V}{R} = \frac{0.228}{20,000} = \underline{\underline{1.1 \times 10^{-5} \text{ A}}}$

3. a) $Q = V \times C = 6 \times (2.2 \times 10^{-6}) = \underline{\underline{1.3 \times 10^{-5} \text{ C}}}$

$E = \frac{1}{2} CV^2 = \frac{1}{2} \times (2.2 \times 10^{-6}) \times 6^2 = \underline{\underline{4.0 \times 10^{-5} \text{ J}}}$

b) $V = V_0 e^{-\frac{t}{RC}}$
 $= 6 \times e^{-\frac{0.5}{0.22}} \text{ C}$
 $= \underline{\underline{0.62 \text{ V}}}$
 $R \times C = 100 \times 10^3 \times 2.2 \times 10^{-6} = \underline{\underline{0.22 \text{ seconds}}}$

c) $E = \frac{1}{2} CV^2 = \frac{1}{2} (2.2 \times 10^{-6}) \times 0.62^2$
 $= \underline{\underline{4.23 \times 10^{-7} \text{ J}}}$

4. a) $I = V/R = 12/200 = \underline{\underline{0.06A}}$

ii) $E = \frac{1}{2} CV^2 = \frac{1}{2} \times (4.7 \times 10^{-6}) \times 12^2 = \underline{\underline{0.0034J}}$

b) $\frac{V}{V_0} = e^{-t/R}$
 $\frac{3}{12} = e^{-\frac{t}{1.034}}$ $R/C = 220 \times 10^3 \times 4.7 \times 10^{-6} = \underline{\underline{1.034 \text{ seconds}}}$

$\ln\left(\frac{3}{12}\right) = \frac{-t}{1.034} \rightarrow t = \ln 0.25 \times 1.034 = \underline{\underline{1.43s}}$

c) $E = E_{\text{initial}} - E_{\text{final}} = \overset{(4. a ii)}{0.0034} - \frac{1}{2} CV^2$
 $= 0.0034 - \frac{1}{2} (4.7 \times 10^{-6}) \times 3^2 = \underline{\underline{0.00319J}}$

23.4 Dielectrics

1. a) $C = \frac{A \epsilon_0 \epsilon_r}{d}$ i) Dielectric $\rightarrow \epsilon_r$ increases, so C increases
 ii) $Q = VC$, so as C increases, Q increases

b) $E = \frac{1}{2} QV$, so if Q increases, E increases.

2. Circuit broken, so no current and Q stays the same
 $E = \frac{1}{2} \frac{Q^2}{C}$, as dielectric is removed C decreases (see above)
 So E must increase.

$\hookrightarrow$ work done to overcome electrostatic attraction between charges on dielectric surface and plates.

3. a) $C = \frac{A \epsilon_0 \epsilon_r}{d} \rightarrow$ all constant apart from ϵ_r now 7.0
 C with $\epsilon_r = 1$ is 1.4 pF, so $\times 7 = \underline{\underline{9.8 pF}}$

b) $E = \frac{1}{2} CV^2 = \frac{1}{2} \times (9.8 \times 10^{-14}) \times 15^2 = \underline{\underline{1.103 \times 10^{-9} J}}$ or 1.1 nJ

4. b) ~~$C = \frac{A \epsilon_0 \epsilon_r}{d}$~~
 a) $E = \frac{V}{d}$ $d = \frac{V}{E} = \frac{100}{700 \times 10^6} = \underline{\underline{1.43 \times 10^{-7} m}}$
 $E = \frac{1}{2} CV^2 = 0.5 \times (100 \times 10^{-3}) \times 100^2 = 500 J$
 b) volume = $1.6 \times 1.43 \times 10^{-7} = 2.28 \times 10^{-7}$ $E \text{ per V} = \frac{500}{2.28 \times 10^{-7}} = \underline{\underline{2.18 \text{ MJ m}^{-3}}}$